

## Exercise Set 3

**Exercise 3.1.** Assume unit  $B_2$ -circuit-delay and zero wire-delay.

- (a) Show that for  $n$  inputs with arrival times  $t_i \in \mathbb{N}$  ( $i = 1, \dots, n$ ) there are  $n$ -ary AND, OR or XOR circuits over  $B_2$  with delay  $d \in \mathbb{N}$  if and only if

$$\sum_{i=1}^n 2^{t_i-d} \leq 1.$$

- (b) Provide an algorithm that finds such a circuit in  $\mathcal{O}(n \log n)$  time.

(3 + 3 points)

**Exercise 3.2.** Consider a prefix tree computing  $z_n \circ \dots \circ z_1$  for generate/propagate pairs  $z_1, \dots, z_n$  with arrival times  $t_1, \dots, t_n \in \mathbb{N}$ , where  $\circ$  is the prefix operator for adder circuits. Let  $F_k$  be the first Fibonacci number that is at least as large as  $\sum_{i=1}^n (F_{t_i+3} - 1)$ .

- (a) Show that a prefix tree with  $B_2$  delay at most  $k$  can be computed by computing a prefix tree for an instance with modified arrival times  $t'_1, \dots, t'_n \in \mathbb{N}$  with  $\max\{t'_i : 1 \leq i \leq n\} \leq 2n - 1$ .
- (b) Assume linear-time addition and multiplication with constants. Show that for any fixed  $\gamma > 1$  a prefix carry bit circuit with  $B_2$ -delay at most

$$\log_{\varphi} \left( \sum_{i=1}^n \varphi^{t_i} \right) + 4 + 2.1 \cdot n^{1-\gamma}$$

can be found in  $\mathcal{O}(n\gamma \log^2 n)$  time where  $\varphi$  is the golden ratio.

(2 + 5 points)

**Exercise 3.3.** Let  $n = 2^k$  for  $k \in \mathbb{N}$  and  $a, b$  two  $n$ -bit numbers representing  $|a|, |b| \in \mathbb{N}$ . Define  $f^n \in B_{2n, 2n}$  as  $f^n(a, b) := |a| \cdot |b|$  i.e. the product of two naturals.

- (a) A *bit-shift* is a multiplication by  $2^i$  for  $i \in \mathbb{N}$ . Show that  $|a| \cdot |b|$  can be expressed in terms of at most 3 non-bit-shift multiplications of  $\frac{n}{2}$ -bit numbers, 6 additions of  $2n$ -bit numbers, and several bit-shifts.
- (b) Show  $S(n) \leq 3 \cdot S(\frac{n}{2}) + cn$  and  $D(n) \leq D(\frac{n}{2}) + d \cdot \log_2 n$  for constants  $c$  and  $d$ .
- (c) Let  $\Omega := \{\wedge, \vee, \oplus\}$ . Show  $S_\Omega(f^n) = \mathcal{O}(n^{\log_2 3})$  and  $D_\Omega(f^n) = \mathcal{O}(\log_2^2 n)$  for circuits with fanout 2.

(1 + 3 + 3 points)

**Deadline:** May 11<sup>th</sup>, before the lecture. The websites for lecture and exercises can be found at

<http://www.or.uni-bonn.de/lectures/ss17/chipss17.html>

In case of any questions feel free to contact me at [ochsendorf@or.uni-bonn.de](mailto:ochsendorf@or.uni-bonn.de).